
 


L02:

(1) Linear Delay Model

 

Tend to use inverter as standard Linear delay model. P/N ratio of unit inverter is 2:1. due to the speed of PMOS is faster than NMOS. and in CMOS we want the speed of PMOS & NMOS equal.

$C_{int}$ : Intrinsic Capacitance of the Model, from PMOS & NMOS


$C_L$ : Load capacitance, from wire and gate capacitance of next logic circuitry.

$$C_d: 2 \cdot C_{unit} \quad C_n: 1 \cdot C_{unit}$$

$$\begin{aligned} \text{Delay} &= k R_w (C_{int} + C_L) = k R_w C_{int} + k R_w C_L \\ &= k R_w C_{int} (1 + C_L / C_{int}) \\ &= \text{Delay (Internal)} + \text{Delay (Load)} \end{aligned}$$
 
## Some derivations of Linear Delay Model


A unit inverter driving  $m$  identical unit inverters



$$\text{Delay} \approx \underbrace{R \cdot 3C_u}_{C_{int}} + \underbrace{m \cdot R \cdot 3C_u}_{C_L}$$

$$\approx 3RC_u + 3mRC_u$$

Driver sized  $W$  times unit size

 

\* Recall two important equations:

$$R = \rho \cdot \frac{L}{W}$$

$$C = \epsilon \cdot \frac{A}{d}$$

Size up driver means we size up  $W$  (width), because  $L$  is fixed by fab tech


So, size up  $W$  times.  $R \downarrow = \frac{R}{W}$   $C \uparrow = W \cdot C$

$$\text{Delay} \approx 3C_u \cdot W \cdot \frac{R}{W} + \frac{R}{W} \cdot 3C_u \cdot m$$

$$\approx 3C_u \cdot R + \frac{m \cdot R \cdot 3C_u}{W}$$

So, sizing up driver actually doesn't effect intrinsic delay, it minimized load delay

- Fan out - of - 4 (FO4)

 

FO4 is standard data, will be provided by the fab vendor to give you a taste of their current process standard speed.

$$\text{Delay} \approx R \cdot 3C_u + 4 \cdot R \cdot 3C_u$$

$$\approx 5 \cdot (R \cdot 3C_u)$$

→ We refer  $R \cdot 3C_u$  as  $\tau$ , a timing constant, as a delay unit to simplify delay analysis.

② Delay in a logic gate.

Delay has two components:

$$d = f + p.$$

$$f = g \cdot h$$

$f$ : effort delay (a.k.a. stage effort)

$g$ : logical effort


• Measures relative ability of gate to deliver current

•  $g = 1$  for inverter

$h$ : electrical effort =  $\frac{C_{out}}{C_{in}}$

- Ratio of output to input capacitance
- Sometimes  $h$  refer as "fanout"

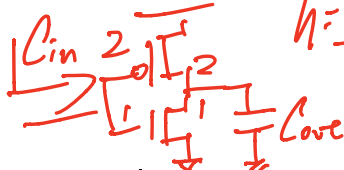F.X.  $h = \frac{2f1}{2f2} = 1$  (Unit inverter)



- $\tau$ : parasitic delay
- Represents delay of gate driving no load
  - Set by internal parasitic capacitance

## Catalog of Gates


- Parasitic delay of common gates
  - In multiples of  $p_{inv}$  ( $\approx 1$ )

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1	<hr/>			
NAND		2	$9/3 = 3$		$n$
NOR		2			$n$
Tristate / mux	2	4			$2n$

10
 
## Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort:  $g = 1$   
 Electrical Effort:  $h = C_{out}/C_{in} = \frac{4 \cdot C_m}{C_m} = 4$   
 Parasitic Delay:  $p = 1$   
 Stage Delay:  $d = g \cdot h + p = 4 \cdot 1 + 1 = 5$   
 $\therefore F_{o4} = 15RC, d_{obs} = d \cdot 4 = 3RC, d = 15RC.$

11

## Multistage Delays

- Path Effort Delay : *the absolute delay.*  $D_F = \sum f_i$
- Path Parasitic Delay  $P = \sum p_i$
- Path Delay  $D = \sum d_i = D_F + P$

12


## Multistage Logic Networks

- Logical effort generalizes to multistage networks

- Path Logical Effort  $G = \prod g_i$


- Path Electrical Effort  $H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$

 - Path Effort  $F = \prod f_i = \prod g_i h_i$



13

## Branching

 

Without branching:  $h_1 h_2 = H$

With branching:  $h_2 = \frac{C_3}{C_2}$

$$h_1 = \frac{3C_2}{C_1}$$

$$h_1 h_2 = 3H$$

Need to account for branching!

$$b_i = \frac{C_{on-path} + C_{off-path}}{C_{on-path}} \quad \rightarrow \quad \begin{aligned} C_{on-path,2} &= C_2 \\ C_{off-path,2} &= 2C_2 \\ b_2 &= \frac{3C_2}{C_2} = 3 \end{aligned}$$

14

## Equivalent Path Efforts

$$H = \frac{C_{out}}{C_{in}}$$

$$B = \prod b_i$$

$$BH = \prod h_i$$

$$G = \prod g_i$$

$$P = \sum p_i$$

Path Effort

$$F = GBH = \prod g_i h_i$$

- Path Effort

- Does not change with added inverters
- Does not depend on sizes, but on topology

15

## Method of Logical Effort

- |                                   |  |
|-----------------------------------|--|
| 1) Compute path effort            | $F = GBH$                                  |
| 2) Estimate best number of stages | $N = \log_4 F$                             |
| 3) Sketch path with N stages      |  |
| 4) Estimate least delay           | $D = NF^{\frac{1}{N}} + P$                 |
| 5) Determine best stage effort    | $\hat{f} = F^{\frac{1}{N}}$                |
| 6) Find gate sizes                | $C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$ |

28

## Summary

- Logical effort is useful for thinking of delay in circuits
  - Numeric logical effort characterizes gates
  - Paths are fastest when effort delays are  $\sim 4$
  - Path delay is weakly sensitive to stages, sizes
  - But using fewer stages doesn't mean faster paths
  - Delay of path is about  $\log_4 F$  FO4 inverter delays
  - Inverters and NAND2 best for driving large caps
- Provides language for discussing fast circuits
  - But requires practice to master
- Next lecture – process variations

29